

# Experimental Methods

## Lecture 23

November 11<sup>th</sup>, 2020

# Two-port networks


- A linear two-port network is a system with multiple inputs and multiple outputs.



- This system is linear and time invariant. It constitutes a more accurate scheme for a measurement instrument, *as it also includes the perturbation that a measurement device exerts on the physical system at its input.*
- two-port networks need not to be passive, and may actively increase the physical energy of signals going through them. The most classical example are electrical active two-port devices, like voltage and/or current amplifiers.
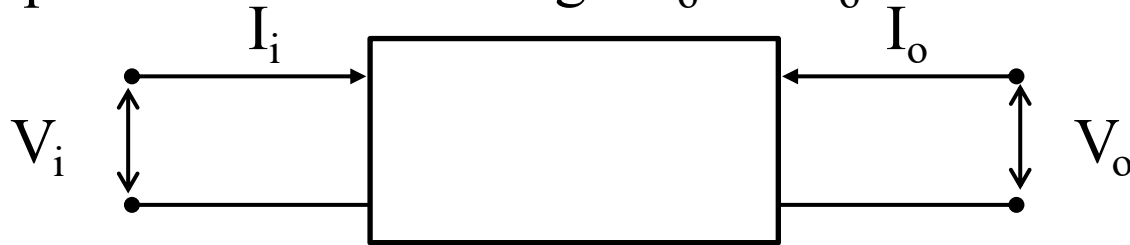
# The voltage amplifier

- The device is constituted by two ports. In each port we find two signals:
  - The input current and voltage  $I_i$  and  $V_i$
  - The output current and voltage  $V_o$  and  $I_o$




- In the frequency domain, as the system is linear, we can write, (for instance)

$$\begin{aligned} I_i &= V_i / Z_i + G_{io} I_o \\ V_o &= G_{oi} V_i + Z_o I_o \end{aligned} \rightarrow \begin{pmatrix} I_i \\ V_o \end{pmatrix} = \begin{pmatrix} 1/Z_i & G_{io} \\ G_{oi} & Z_o \end{pmatrix} \cdot \begin{pmatrix} V_i \\ I_o \end{pmatrix}$$

- $Z_i$  is called input impedance,  $Z_o$  output impedance, and non diagonal coefficients are often called gains.

# The voltage amplifier

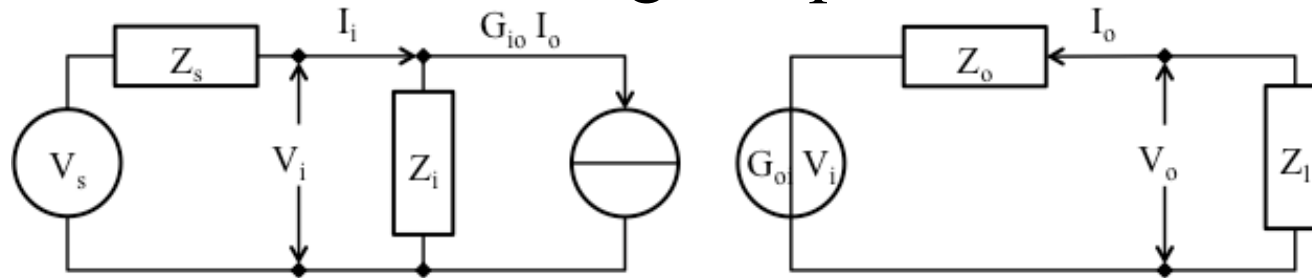


- Adding the new branches, these are now the circuit equations:

$$I_i = \frac{V_i}{Z_i} + G_{io} I_o \quad V_o = G_{oi} V_i + Z_o I_o \quad I_i = \frac{V_s - V_i}{Z_s} \quad V_o = -Z_L I_o$$

- These can now be solved in the general case.
- We are however interested in the limiting case (ideal amplifier) in which,  $Z_i \rightarrow \infty$  and  $Z_L \rightarrow \infty$ . Then

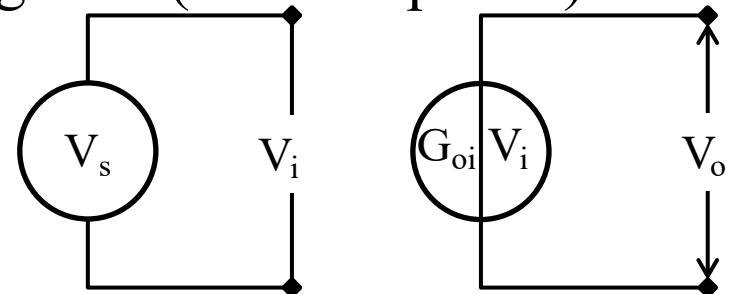
$$I_o = -\frac{V_o}{Z_L} \rightarrow 0 \quad I_i = \frac{V_i}{Z_i} - \frac{G_{io} V_o}{Z_L} \rightarrow 0$$




$$V_i = V_s - Z_s I_i \rightarrow V_s \quad V_o = G_{oi} V_i - \frac{Z_o}{Z_L} V_o \rightarrow G_{oi} V_i = G_{oi} V_s$$
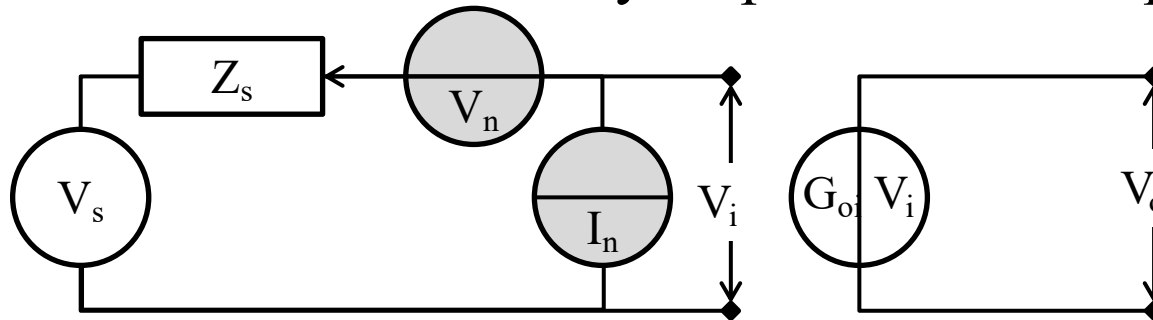
# Noise in two port systems: voltage amplifier

- Thus, in conclusion the ideal noisy amplifier can be represented as




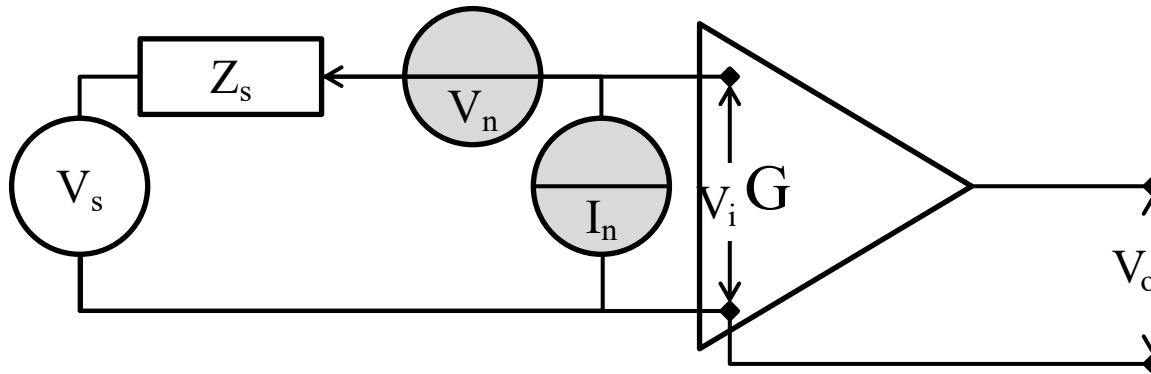- Or, with a different graphics, and the simpler symbol  $G$  for the gain, as



- As the output voltage is  $V_o = G(V_s + V_n + I_n Z_s)$  noise can be expressed at input as  $V_n^{\text{in}} = V_n + I_n Z_s$
- Notice that  $I_n$  truly circulate within  $Z_s$ . Thus the amplifier perturbs the source. This perturbation is often called the amplifier *back-action*
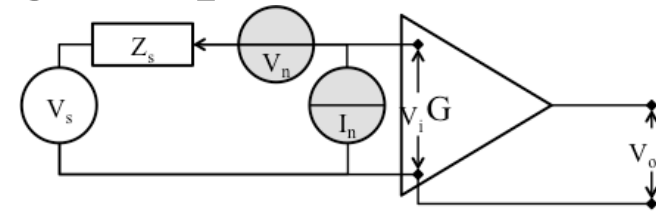
# Noise in two port systems: voltage amplifier



- In summary the noise at input of an ideal, noisy amplifier is  $V_n^{\text{in}} = V_n + I_n Z_s$
- Now remember
  - If  $z(t) = \alpha x(t) + \beta y(t)$
  - Then  $S_{z,z}(\omega) = \alpha^2 S_{x,x}(\omega) + \beta^2 S_{y,y}(\omega) + 2\alpha\beta \text{Re}\{S_{x,y}(\omega)\}$
- Then

$$S_{V_n^{\text{in}}, V_n^{\text{in}}}(\omega) = S_{V_n, V_n}(\omega) + |Z_s(\omega)|^2 S_{I_n, I_n} + 2\text{Re}\{S_{V_n, Z_s I_n}(\omega)\}$$

- Furthermore

$$\begin{aligned} R_{V_n, Z_s I_n}(\tau) &= \left\langle \int_0^\infty Z_s(t') I_n(t + \tau - t') V_n(t) dt' \right\rangle = \\ &= \int_0^\infty Z_s(t') \langle I_n(t + \tau - t') V_n(t) \rangle dt' = \int_0^\infty Z_s(t') R_{V_n, I_n}(\tau - t') dt' \end{aligned}$$

- Then


$$S_{V_n, Z_s I_n}(\omega) = Z_s(\omega) S_{V_n, I_n}(\omega)$$

- And

$$S_{V_n^{\text{in}}, V_n^{\text{in}}}(\omega) = S_{V_n, V_n}(\omega) + |Z_s(\omega)|^2 S_{I_n, I_n} + 2\text{Re}\{Z_s(\omega) S_{V_n, I_n}(\omega)\}$$
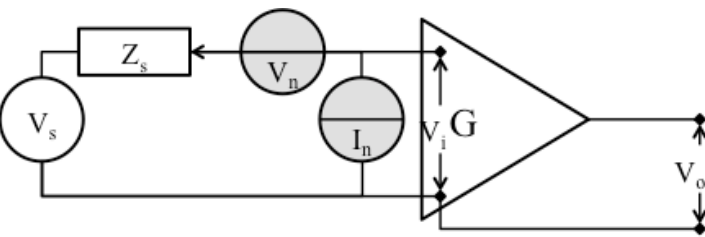
# Critical noise parameters for a 2-port device

- Noise at input  $V_n^{\text{in}} = V_n + I_n Z_s$
- Before proceeding further let's give a few important definitions:
  1. Noise energy or temperature  $E_n(\omega) = k_B T_n(\omega) \equiv \sqrt{S_{V_n V_n}(\omega) S_{I_n I_n}(\omega)}$
  2. Noise Resistance  $R_n(\omega) \equiv \sqrt{S_{V_n V_n}(\omega) / S_{I_n I_n}(\omega)}$
  3. Noise cross-coherence  $\rho_n(\omega) = S_{V_n I_n}(\omega) / \sqrt{S_{V_n V_n}(\omega) S_{I_n I_n}(\omega)}$
- Inverting these definitions
  1. Voltage PSD:  $S_{V_n V_n}(\omega) = k_B T_n(\omega) R_n(\omega)$
  2. Current PSD  $S_{I_n I_n}(\omega) = k_B T_n(\omega) / R_n(\omega)$
  3. Voltage-current cross spectrum  $S_{V_n I_n}(\omega) = k_B T_n(\omega) \rho_n(\omega)$



# Noise in a voltage amplifier

- From previous page

$$S_{V_n V_n}(\omega) = k_B T_n(\omega) R_n(\omega); S_{I_n I_n}(\omega) = \frac{k_B T_n(\omega)}{R_n(\omega)}; S_{V_n I_n}(\omega) = k_B T_n(\omega) \rho_n(\omega)$$

- Total PSD at input, is given by

$$S_{V_n^{in} V_n^{in}}(\omega) = S_{V_n V_n}(\omega) + |Z_s(\omega)|^2 S_{I_n I_n}(\omega) + 2 \operatorname{Re}\{Z_s(\omega) S_{V_n I_n}(\omega)\}$$

becomes, by substituting the definition above:


$$S_{V_n^{in} V_n^{in}}(\omega) = k_B T_n(\omega) \left[ R_n(\omega) + |Z_s(\omega)|^2 / R_n(\omega) + 2 \operatorname{Re}\{Z_s(\omega) \rho_n(\omega)\} \right]$$

Voltage noise depends on the impedance of the source and on that of noise


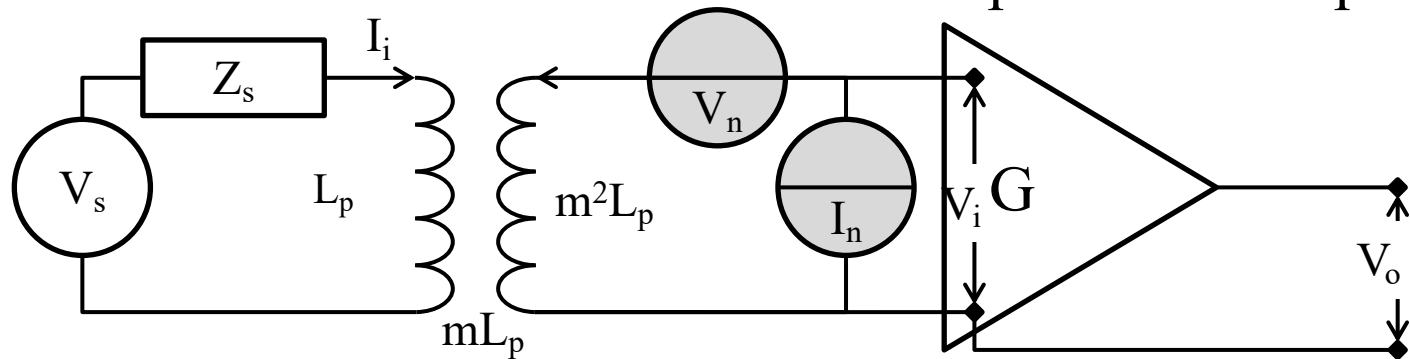
# Adjusting noise resistance

- Now we want to show that, at least to some approximation, the noise resistance can be adjusted without affecting the noise temperature. To do this, put an m-turns ideal transformer at the input of our amplifier:



- You can calculate that :

$$V_s = I_i(Z_s + sL_p) + m sL_p I_n = 0 \quad V_i = s m L_p I_i + s m^2 L_p I_n + V_n$$

$$I_i = \frac{V_s - m sL_p I_n}{Z_s + sL_p} \quad V_i = s m L_p \frac{V_s - m sL_p I_n}{Z_s + sL_p} + s m^2 L_p I_n + V_n$$

$$V_i = \frac{s m L_p}{Z_s + sL_p} \left( V_s - (m s L_p + Z_s m + m s L_p) I_n + \frac{V_n Z_s + sL_p}{m} \right)$$

# Adjusting noise resistance

- From

$$I_i = \frac{V_s - m s L_p I_n}{Z_s + s L_p}$$

$$V_i = \frac{s m L_p}{Z_s + s L_p} \left( V_s - (m s L_p + Z_s m + m s L_p) I_n + \frac{V_n Z_s + s L_p}{m} \right)$$


- Finally

$$I_i = \frac{V_s - m s L_p I_n}{Z_s + s L_p} V_i = \frac{s m L_p}{Z_s + s L_p} \left( V_s + Z_s (-m I_n) + \frac{V_n Z_s + s L_p}{m} \right)$$

- Now make  $|s L_p| \gg |Z_s|$


$$I_i = -m I_n \quad V_i = m \left( V_s + Z_s (-m I_n) + \frac{V_n}{m} \right)$$

- Then the situation looks like this:

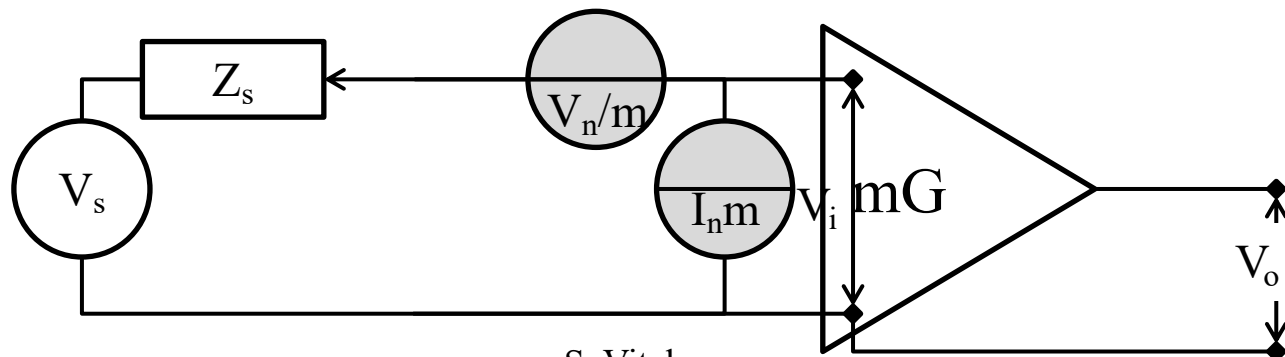
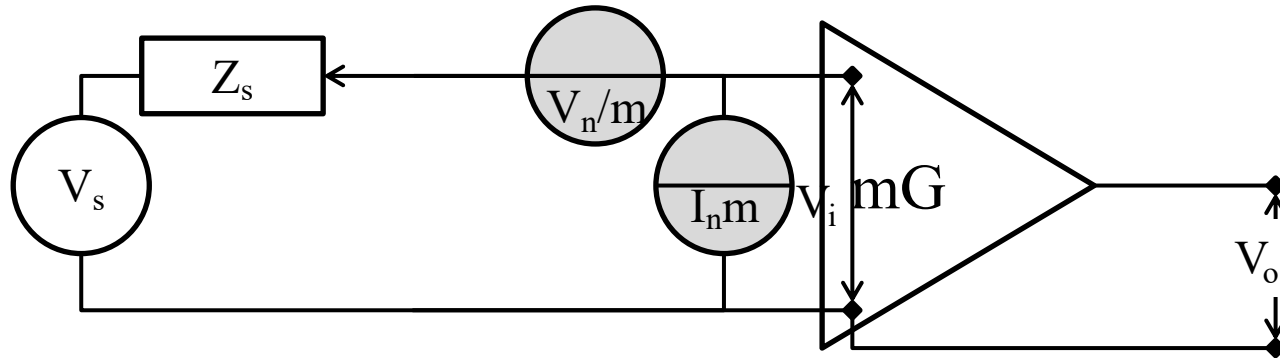
# Adjusting noise resistance

- The equivalent noise at input consists of a current noise  $I_n' = I_n m$  and voltage noise  $V_n' = V_n / m$ .



- The new noise parameters are then

$$k_B T_n'(\omega) \equiv \sqrt{\frac{S_{V_n V_n}(\omega)}{m^2}} m^2 S_{I_n I_n}(\omega) = k_B T_n(\omega)$$

$$R_n'(\omega) \equiv \sqrt{\frac{S_{V_n V_n}(\omega)}{m^2}} / S_{I_n I_n}(\omega) m^2 = \frac{R_n(\omega)}{m^2}$$

$$\rho_n'(\omega) = \rho_n(\omega)$$

# Minimizing noise by impedance matching

- Total noise PSD at input, at a given frequency

$$S_{V_n^{\text{in}} V_n^{\text{in}}}(\omega) = k_B T_n(\omega) \left[ R_n(\omega) + |Z_s(\omega)|^2 / R_n(\omega) + 2 \operatorname{Re} \{ Z_s(\omega) \rho_n(\omega) \} \right]$$

- Can be minimized by adjusting  $R_n$

$$\partial S_{V_n^{\text{in}} V_n^{\text{in}}}(\omega) / \partial R_n(\omega) = k_B T_n(\omega) \left[ 1 - |Z_s(\omega)|^2 / R_n^2(\omega) \right] = 0$$

- That gives  $R_n(\omega) = |Z_s(\omega)|$
- When this condition is fulfilled the contribution of voltage noise and of current noise become equal and the PSD becomes

$$S_{V_n^{\text{in}} V_n^{\text{in}}}(\omega) = 2k_B T_n(\omega) \left[ |Z_s(\omega)| + \operatorname{Re} \{ Z_s(\omega) \rho_n(\omega) \} \right]$$


- Or, for uncorrelated generators

$$S_{V_n^{\text{in}} V_n^{\text{in}}}(\omega) = 2k_B T_n(\omega) |Z_s(\omega)|$$

- Watch out! This is not Nyquist law, and  $T_n$  is not  $T$
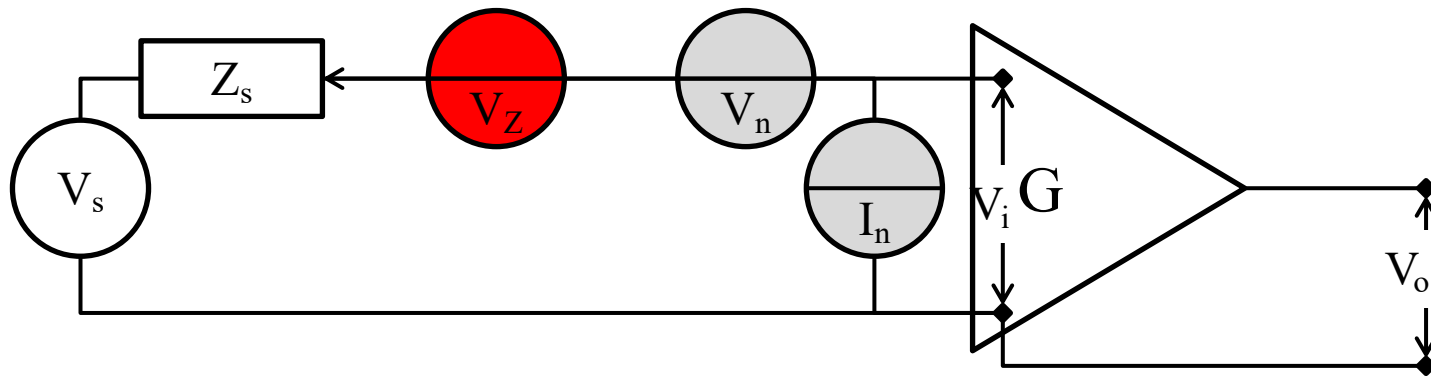
# Noise figure and matched source

- We want to discuss now another noise minimization that achieves a similar result, but in term of source impedance.
- If the source impedance has a real part, at thermal equilibrium it will be noisy, with a noise PSD given by Nyquist formula.



- Total noise at input will then have a PSD (we omit the frequency dependence in order to simplify the writing), given by:

$$S_{V_n^{\text{in}} V_n^{\text{in}}} = k_B T_n \left[ R_n + |Z_s|^2 / R_n + 2 \operatorname{Re} \{ Z_s \rho_n \} \right] + 2 k_B T \operatorname{Re} \{ Z_s \}$$

# Noise figure and matched source

- From the PSD

$$S_{V_n^{\text{in}} V_n^{\text{in}}} = k_B T_n \left[ R_n + |Z_s|^2 / R_n + 2 \operatorname{Re}\{Z_s \rho_n\} \right] + 2k_B T \operatorname{Re}\{Z_s\}$$

- We define the noise figure as the ratio, *measured in decibels*, between the total noise PSD and that of the thermal noise alone

$$F = 20 \operatorname{Log}_{10} \left\{ \frac{k_B T_n \left[ R_n + |Z_s|^2 / R_n + 2 \operatorname{Re}\{Z_s \rho_n\} \right] + 2k_B T \operatorname{Re}\{Z_s\}}{2k_B T \operatorname{Re}\{Z_s\}} \right\}$$

- That is  $F = 20 \operatorname{Log}_{10} \left\{ 1 + \frac{T_n}{T} \left[ \frac{R_n}{2 \operatorname{Re}\{Z_s\}} + \frac{|Z_s|^2}{2 R_n \operatorname{Re}\{Z_s\}} + \frac{\operatorname{Re}\{Z_s \rho_n\}}{\operatorname{Re}\{Z_s\}} \right] \right\}$
- For uncorrelated noise sources this figure has a minimum when

$$Z_s = R_n$$


- Whose value is  $F_{\min} = 20 \operatorname{Log}_{10} \left\{ 1 + \frac{T_n}{T} \right\}$

# A practical example: a popular low-noise instrument amplifier

- From the attached noise figure plot, let's derive noise temperature and noise resistance at 100 Hz, 1 kHz and 10 kHz
- Calculate also the voltage and current PSD
- Notice: one sided PSD are used here



**SR560 Noise Figure**

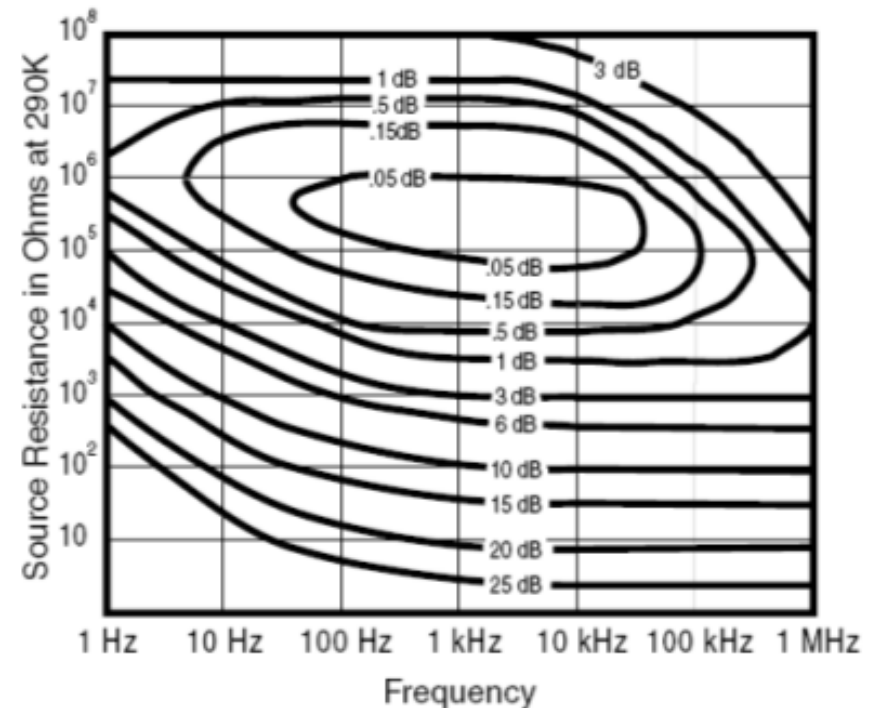


# An experimental example

APPLIED PHYSICS LETTERS 93, 172506 (2008)
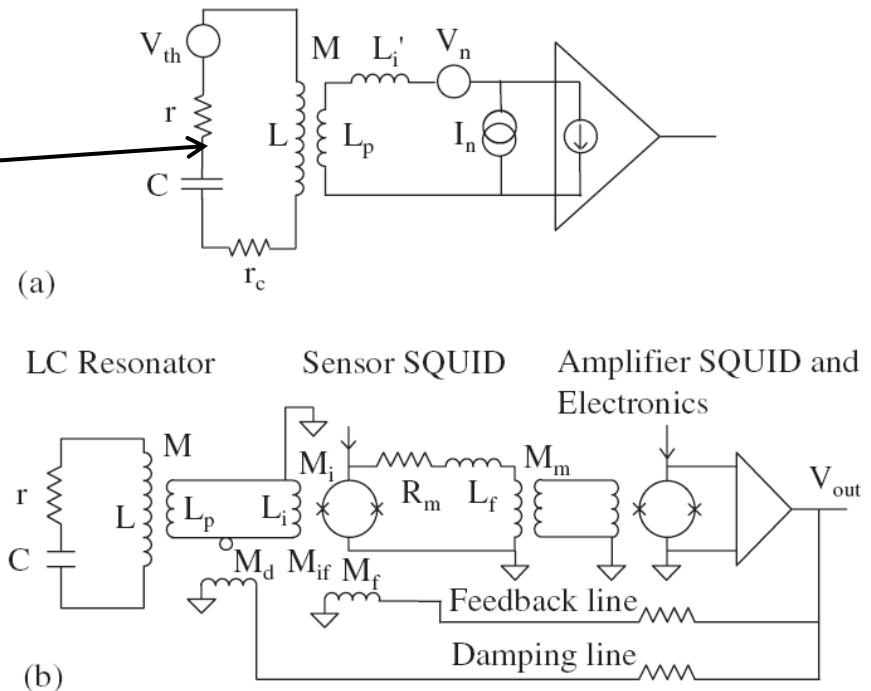
## 10 $\hbar$ superconducting quantum interference device amplifier for acoustic gravitational wave detectors




P. Falferi,<sup>1,2,a)</sup> M. Bonaldi,<sup>1,2</sup> M. Cerdonio,<sup>3,4</sup> R. Mezzena,<sup>5,2</sup> G. A. Prodi,<sup>5,2</sup> A. Vinante,<sup>4</sup> and S. Vitale<sup>5,2</sup>

- Current noise excites the resonant circuit (9 kHz).
- The PSD peak gives a measurement of the current noise
- Outside the resonance range the noise is dominated by voltage noise





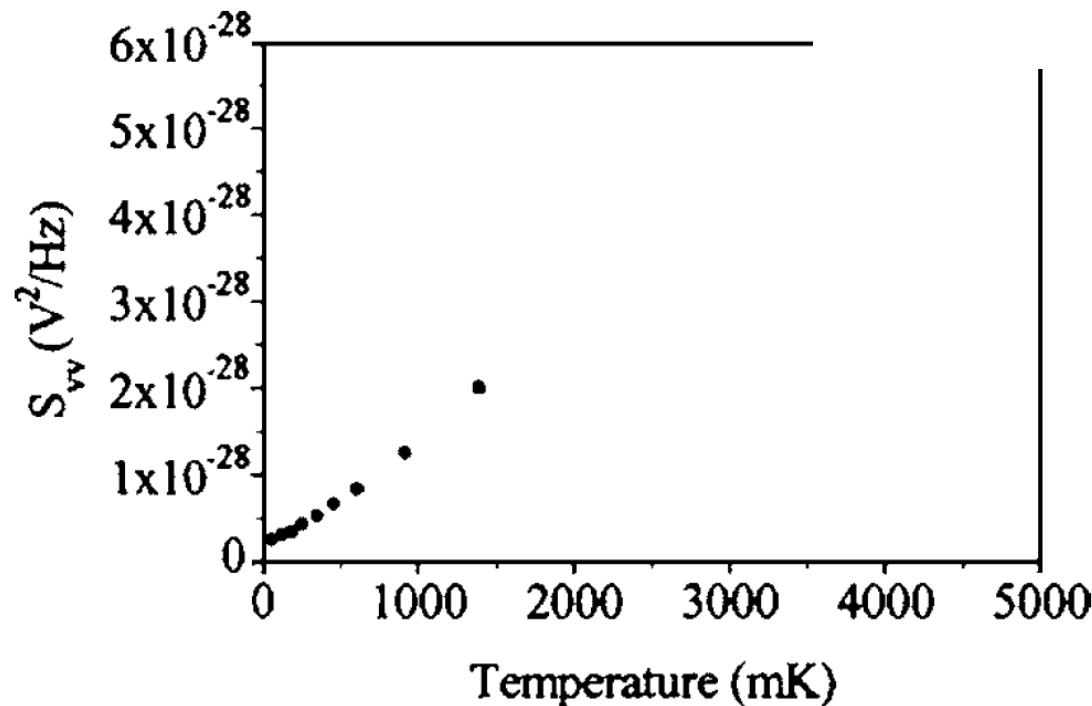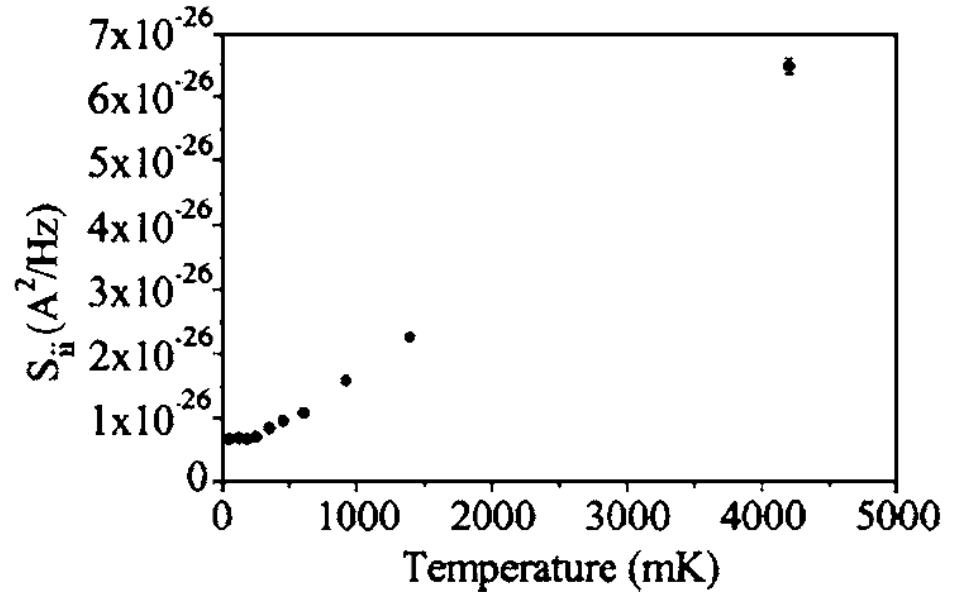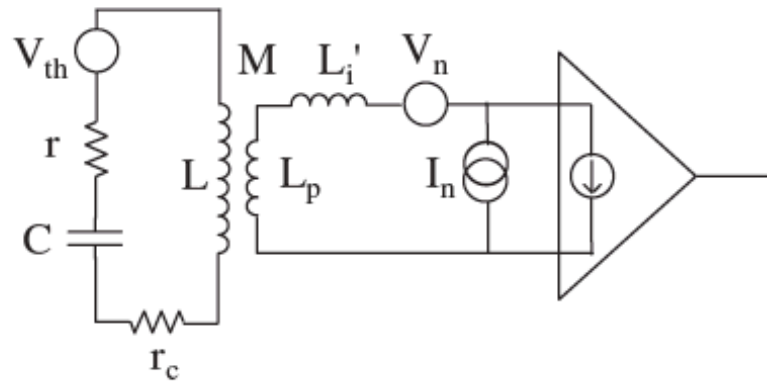
## 27 $\hbar$ SQUID amplifier operating with high-Q resonant input load



Current noise and voltage noise are then independently measured (pictures from a different experiment)
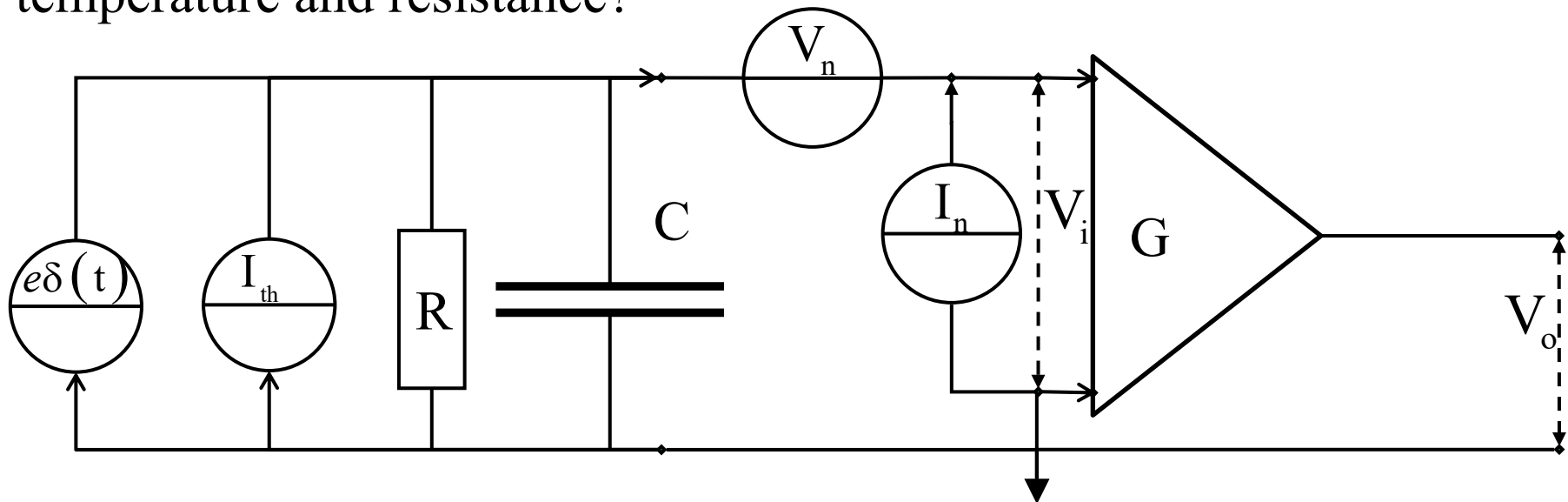
# The meaning of noise energy. One example: charge detector

- A charge detector consisting of a lossy capacitor read out by a low noise amplifier.  $I_{th}$  is the Nyquist current noise generator associated with  $R$ . We will assume  $V_n$  and  $I_n$  to be uncorrelated.
- The signal at input consists of a single charge  $e$ . That is, the signal consists of a current impulse  $I(t)=e\delta(t)$
- What is the minimum measurable value of  $e$ , given the amplifier noise temperature and resistance?




# A short cut

- As the signal is a current, let's work at input, i.e. for current
- Fourier transform of the (unit amplitude) signal  $I(\omega) = 1$
- Let's call  $I'_n = I_n + I_{th}$ .
- Total input due to noise is:  $V_{i,noise} = V_n + ZI'_n$
- As an equivalent current  $I_{n,e} = I'_n + \frac{V_n}{Z}$
- Total equivalent input noise PSD ( $I_n$  and  $V_n$  white and uncorrelated)

$$S_{I_{n,e}I_{n,e}}(\omega) = S_{I'_nI'_n} + \frac{S_{V_nV_n}(1 + \omega^2 R^2 C^2)}{R^2}$$
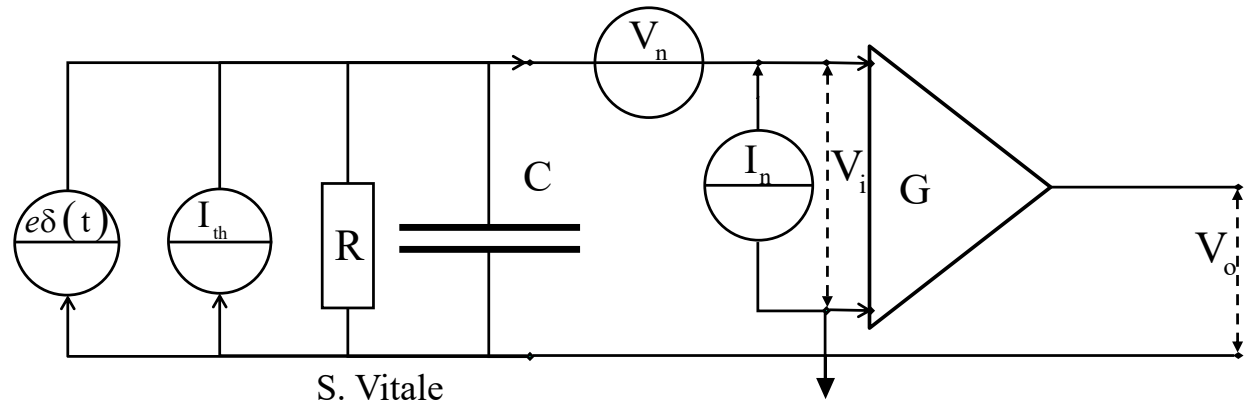
$$S_{I_{n,e}I_{n,e}}(\omega) = S_{I'_nI'_n} + \frac{S_{V_nV_n}}{R^2} + S_{V_nV_n} \omega^2 C^2$$



# A short cut

- Furthermore, from


$$S_{I_{n,e}I_{n,e}}(\omega) = S_{I'_nI'_n} + \frac{S_{V_nV_n}}{R^2} + S_{V_nV_n}\omega^2C^2$$

- We get

$$S_{I_{n,e}I_{n,e}}(\omega) = \left( S_{I'_nI'_n} + \frac{S_{V_nV_n}}{R^2} \right) \left( 1 + \frac{S_{V_nV_n}C^2}{S_{I'_nI'_n} + \frac{S_{V_nV_n}}{R^2}} \omega^2 \right)$$

- or
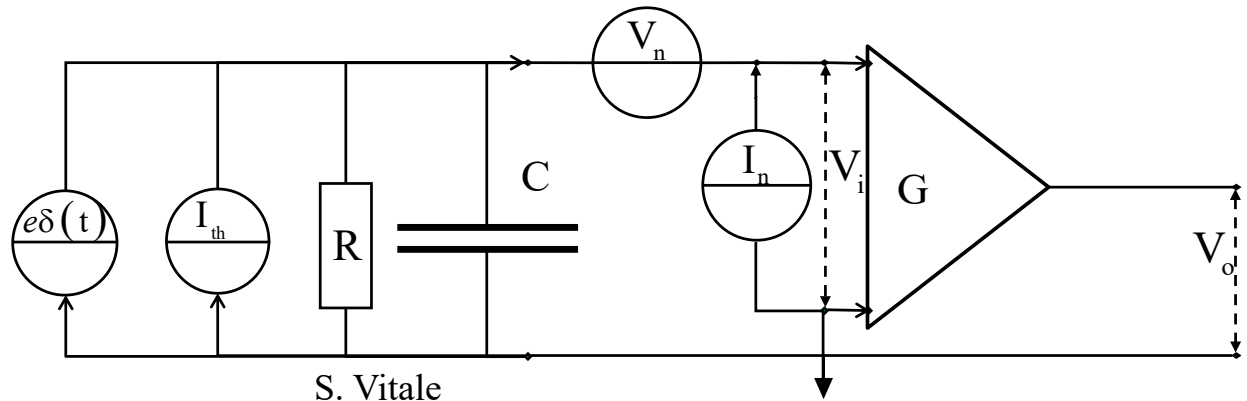
$$S_{I_{n,e}I_{n,e}}(\omega) = S_{I_o}(1 + \tau^2\omega^2)$$



# A short cut

- Thus, signal

$$I(\omega) = 1$$


- Noise

$$S_{I_{n,e}I_{n,e}}(\omega) = S_{I_o}(1 + \tau^2 \omega^2)$$

- Wiener filter error

$$\sigma_e = \left( \frac{1}{2\pi} \int_{-\infty}^{\infty} \frac{1}{S_{I_o}(1 + \omega^2 \tau^2)} d\omega \right)^{-1/2} = \frac{\sqrt{S_{I_o} \tau}}{\sqrt{\frac{1}{2\pi} \int_{-\infty}^{\infty} \frac{1}{1 + x^2} dx}}$$

$$= \sqrt{2S_{I_o} \tau}$$

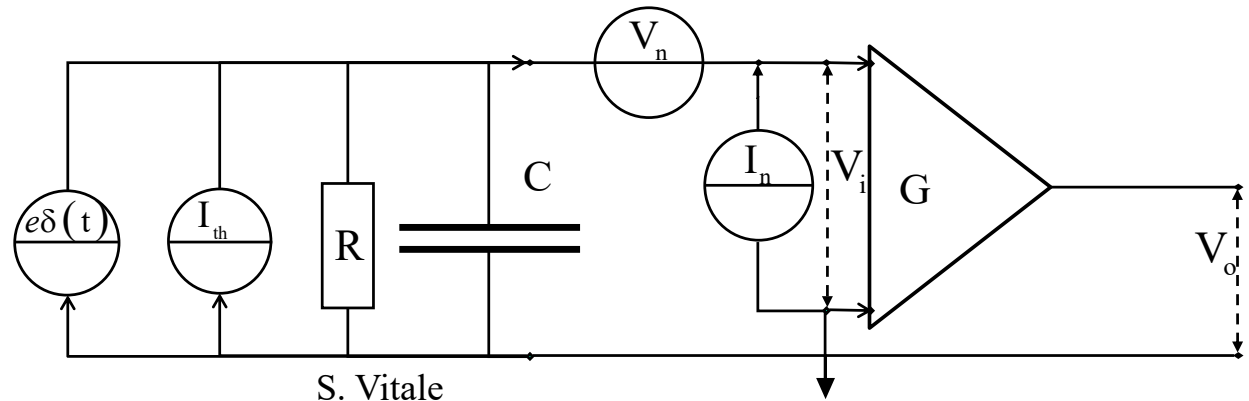

# A short cut

- Thus,

$$\sigma_e = \sqrt{2S_{Io}\tau}$$

- And

$$S_{I_{n,e}I_{n,e}}(\omega) = \left( S_{I'_n I'_n} + \frac{S_{V_n V_n}}{R^2} \right) \left( 1 + \frac{S_{V_n V_n} C^2}{S_{I'_n I'_n} + \frac{S_{V_n V_n}}{R^2}} \omega^2 \right)$$

- with

$$S_{I_{n,e}I_{n,e}}(\omega) = S_{Io}(1 + \tau^2 \omega^2)$$

- Then

$$\sigma_e = \sqrt{2 \left( S_{I'_n I'_n} + \frac{S_{V_n V_n}}{R^2} \right) \sqrt{\frac{S_{V_n V_n} C^2}{S_{I'_n I'_n} + \frac{S_{V_n V_n}}{R^2}}}} = \sqrt{2C} \left( S_{V_n V_n} \left( S_{I'_n I'_n} + \frac{S_{V_n V_n}}{R^2} \right) \right)^{\frac{1}{4}}$$

- Now take the limit for  $R \rightarrow \infty$  (low dissipations)

- Then

$$\sigma_e \rightarrow \sqrt{2C} \sqrt{S_{V_n V_n} S_{I'_n I'_n}} = \sqrt{2 C k_B T'_n}$$

# A short cut

- In conclusion

$$\sigma_e = \sqrt{2 C k_B T'_n}$$


- Now suppose that a charge  $\sigma_e$  is deposited on the capacitor. This will get an energy

$$E = \frac{1}{2} C \sigma_e^2 = k_B T'_n$$

- This is the crucial result: the minimum detectable energy is the noise energy of the amplifier
- Notice that if  $T \rightarrow 0$   $T'_n \rightarrow T_n$  as the thermal noise becomes negligible
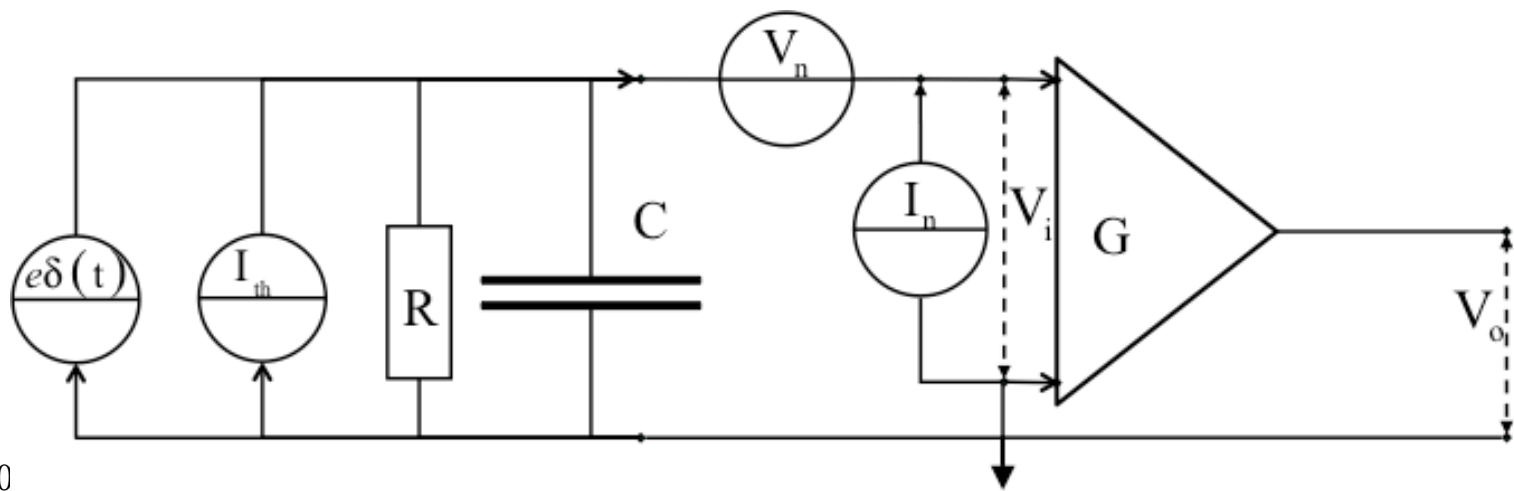
# Example: charge detector

- We answer the question by using optimal filter theory. We are looking in the data for a signal of known shape  $\delta(t)$  and unknown signal amplitude  $e$ .
- Let's then calculate in the frequency domain the signal contribution to  $V_i$ . The Fourier transform of  $I(t)=\delta(t)$  is just  $I(\omega)=1$ . Then
 
$$V_i(\omega) = I(\omega) R (1/i\omega C) / (R + 1/i\omega C) = I(\omega) R / (1 + i\omega CR)$$
- Notice (to be used later)  $V_i(t) = (1/C) e^{-t/RC} \Theta(t)$






# Example: charge detector

- Noise. Let's first calculate transfer functions from generators to  $V_i$ . As usual we do that by considering noise as standard signals. Then

$$V_i = (I_{th} + I_n)R(1/i\omega C)/(R + 1/i\omega C) + V_n = (I_{th} + I_n)R/(1 + i\omega CR) + V_n$$

- As  $I_{th}$  and  $I_n$  are uncorrelated, we can write the PSD as (we omit the frequency dependence of  $T_n$  and  $R_n$ )
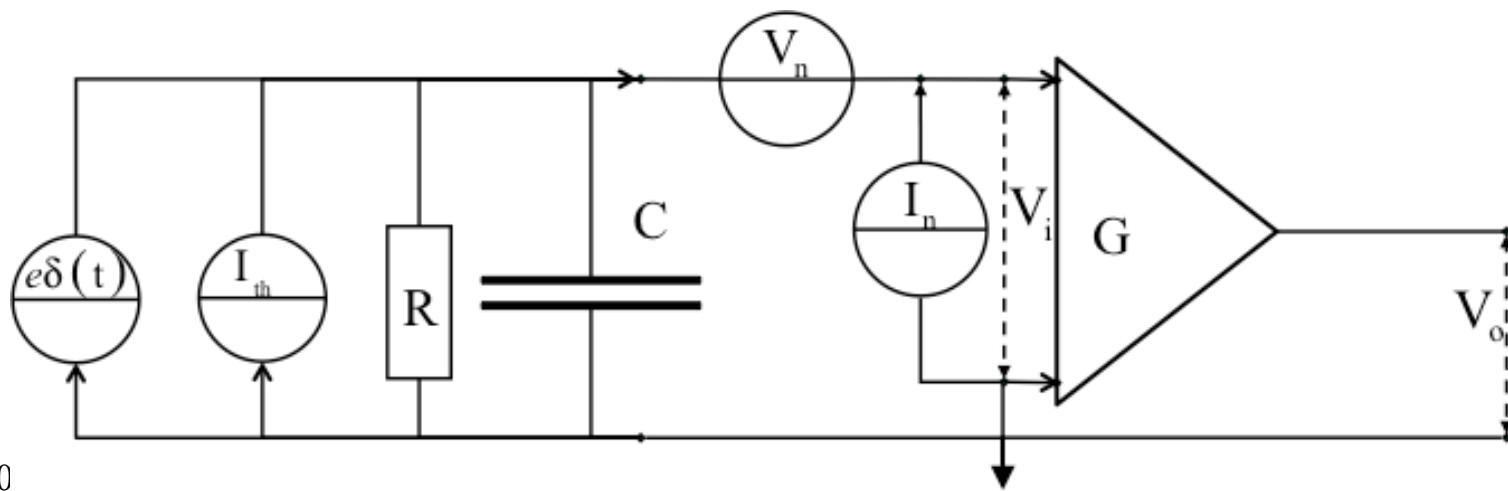
$$S_{V_n^{in}V_n^{in}} = (2k_B T/R + k_B T_n/R_n) \left[ R^2 / (1 + \omega^2 C^2 R^2) \right] + k_B T_n R_n$$



# Example: charge detector

- From signal  $V_i(\omega) = R/(1 + i\omega CR)$
  - And PSD  $S_{V_n^{in}V_n^{in}} = (2k_B T/R + k_B T_n/R_n) [R^2/(1 + \omega^2 C^2 R^2)] + k_B T_n R_n$
  - We calculate the SNR as
- $$SNR = \left[ R^2 / (1 + \omega^2 C^2 R^2) \right] / \left\{ (2k_B T/R + k_B T_n/R_n) [R^2 / (1 + \omega^2 C^2 R^2)] + k_B T_n R_n \right\}$$

- That can be simplified to
- $$SNR = 1 / \left\{ 2k_B T/R + k_B T_n/R_n + k_B T_n R_n (1 + \omega^2 C^2 R^2) / R^2 \right\}$$
- Notice the denominator is the PSD of the noise converted into an input noise current. At this same point the signal is just  $I(\omega)=1$
  - The SNR can be put in a more simple form

$$SNR = \frac{1}{2k_B T/R + k_B T_n/R_n + k_B T_n R_n / R^2 + (k_B T_n / R_n) \omega^2 R_n^2 C^2} = \frac{1}{S_{I_o} (1 + \tau_e^2 \omega^2)}$$

- Where

$$S_{I_o} = (k_B T_n / R_n) \left( 1 + (R_n / R)^2 + (2T / T_n) (R_n / R) \right); \tau_e = R_n C / \sqrt{1 + (R_n / R)^2 + (2T / T_n) (R_n / R)}$$

# Example: charge detector

- According to optimal filter theory, the error on the estimate of the charge  $e$  is given by  $\sigma_e = 1 / \sqrt{(1/2\pi) \int_{-\infty}^{\infty} \text{SNR}(\omega) d\omega}$
- with

$$\text{SNR} = 1 / \left[ S_{\text{Io}} \left( 1 + \tau_e^2 \omega^2 \right) \right]$$

- To perform the calculation, we assume that both  $T_n$  and  $R_n$  are frequency independent then

$$\sigma_e = \sqrt{S_{\text{Io}}} / \sqrt{(1/2\pi) \int_{-\infty}^{\infty} \left( 1 + \tau_e^2 \omega^2 \right)^{-1} d\omega} = \sqrt{2S_{\text{Io}} \tau_e}$$

- Now restore the meaning of symbols:

$$S_{\text{Io}} = k_B T_n / R_n \left( 1 + (R_n / R)^2 + (2T / T_n) (R_n / R) \right); \tau_e = R_n C / \sqrt{1 + (R_n / R)^2 + (2T / T_n) (R_n / R)}$$

- Then  $\sigma_e = \sqrt{2S_{\text{Io}} \tau_e} = \sqrt{2k_B T_n C} \times \sqrt{\sqrt{1 + (R_n / R)^2 + (2T / T_n) (R_n / R)}}$
- Best you can do is when the detector is cold enough and not too lossy

$$(2T / T_n) (R_n / R) \ll 1 \text{ and } (R_n / R) \ll 1$$

- Then  $\sigma_e = \sqrt{2k_B T_n C}$

# Example: charge detector


- In summary the minimum error on the estimate of the charge is

$$\sigma_e = \sqrt{2k_B T_n C}$$

- Now suppose that a charge equal to  $\sigma_e$  is deposited onto the capacitor. This acquires an electrostatic energy.


$$E = \frac{1}{2} \frac{e^2}{C} = \frac{1}{2} \frac{2k_B T_n C}{C} = k_B T_n = E_n$$

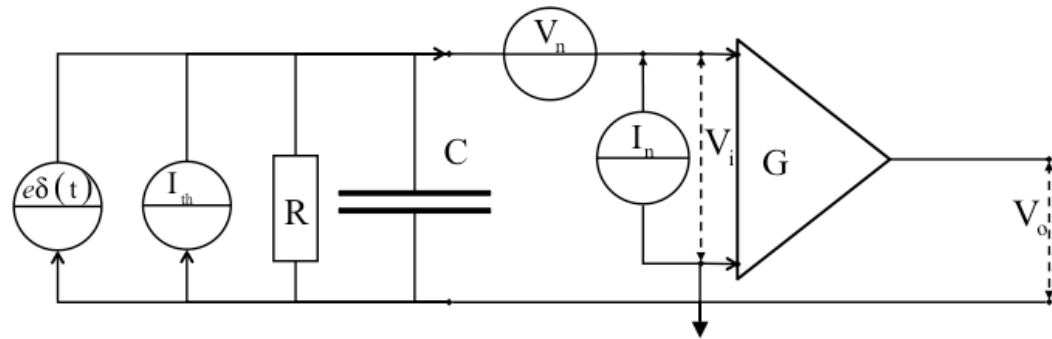- Thus the “minimum detectable charge” (with 100% error) is that depositing an amount of energy equal to the noise energy of the amplifier.*
- This result is valid in general not just for charge detection.



# Further on the example of charge detector

- Equivalent circuit for charge detector

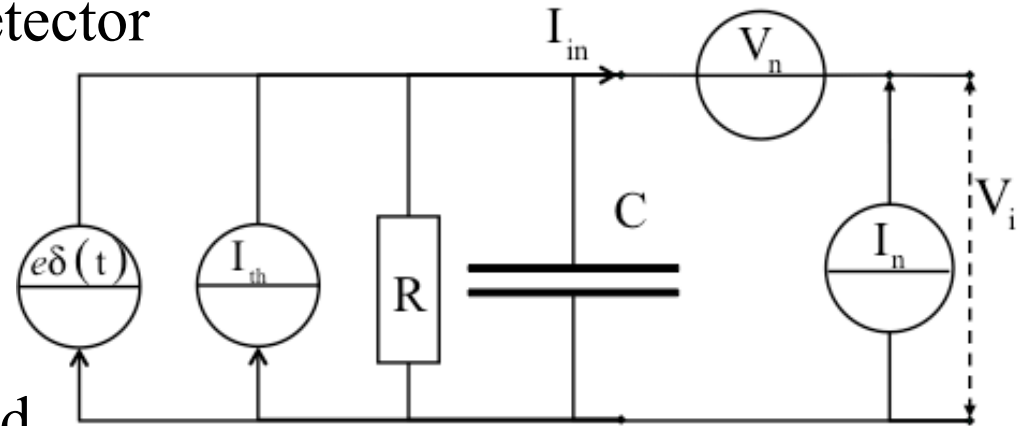

- $V_n$  and  $I_n$  white and uncorrelated
- We can define an effective total current noise  $\tilde{I}_n = I_n + I_{th}$


- With PSD

$$\tilde{S}_{I_n I_n} = \frac{2k_B T}{R} + \frac{k_B T_n}{R_n} \equiv k_B \tilde{T}_n / \tilde{R}_n$$

- and then simplify the circuit as

$$\tilde{T}_n = \sqrt{\left( \frac{2T}{R} + \frac{T_n}{R_n} \right) T_n R_n} = T_n \sqrt{1 + 2 \frac{R_n T}{R T_n}}$$
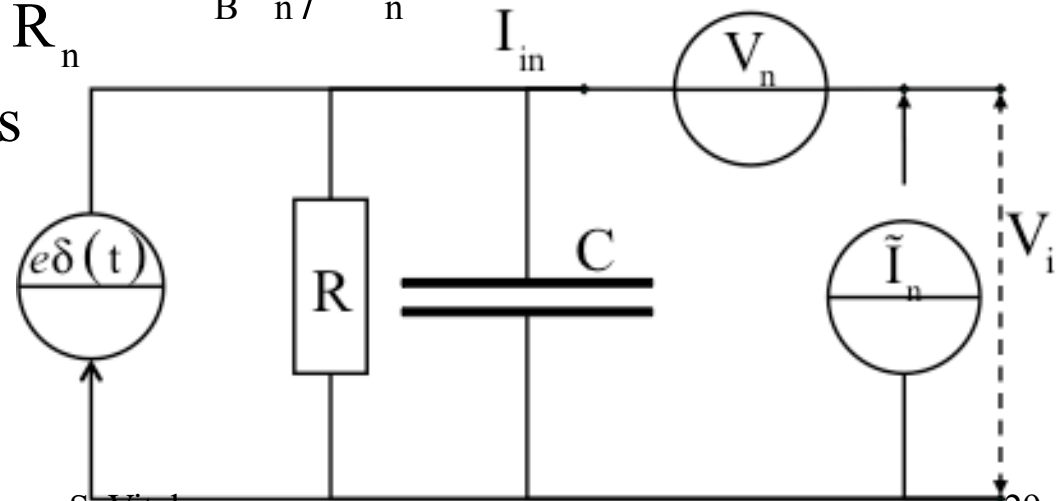
$$\tilde{R}_n = \sqrt{\frac{T_n R_n}{2T/R + T_n/R_n}} = \frac{R_n}{\sqrt{1 + 2(R_n T / R T_n)}}$$




# Total noise at input

- Total equivalent current noise through Z

$$S_{I_{nI_n}} = \frac{2k_B T}{R} + \frac{k_B T_n}{R_n} + \frac{k_B T_n R_n}{R^2} = \frac{2k_B T}{R} + \frac{k_B T_n}{R_n} + \frac{k_B T_n R_n}{R^2} + \frac{k_B T_n R_n}{R^2} \omega^2 R^2 C^2 = S_{Io} (1 + \omega^2 \tau_e^2)$$

$$S_{Io} = \frac{2k_B T}{R} + \frac{k_B T_n}{R_n} + \frac{k_B T_n R_n}{R^2} \quad \tau_e^2 = C^2 R_n^2 \frac{T_n/R_n}{\frac{2T}{R} + \frac{T_n}{R_n} + \frac{T_n R_n}{R^2}}$$

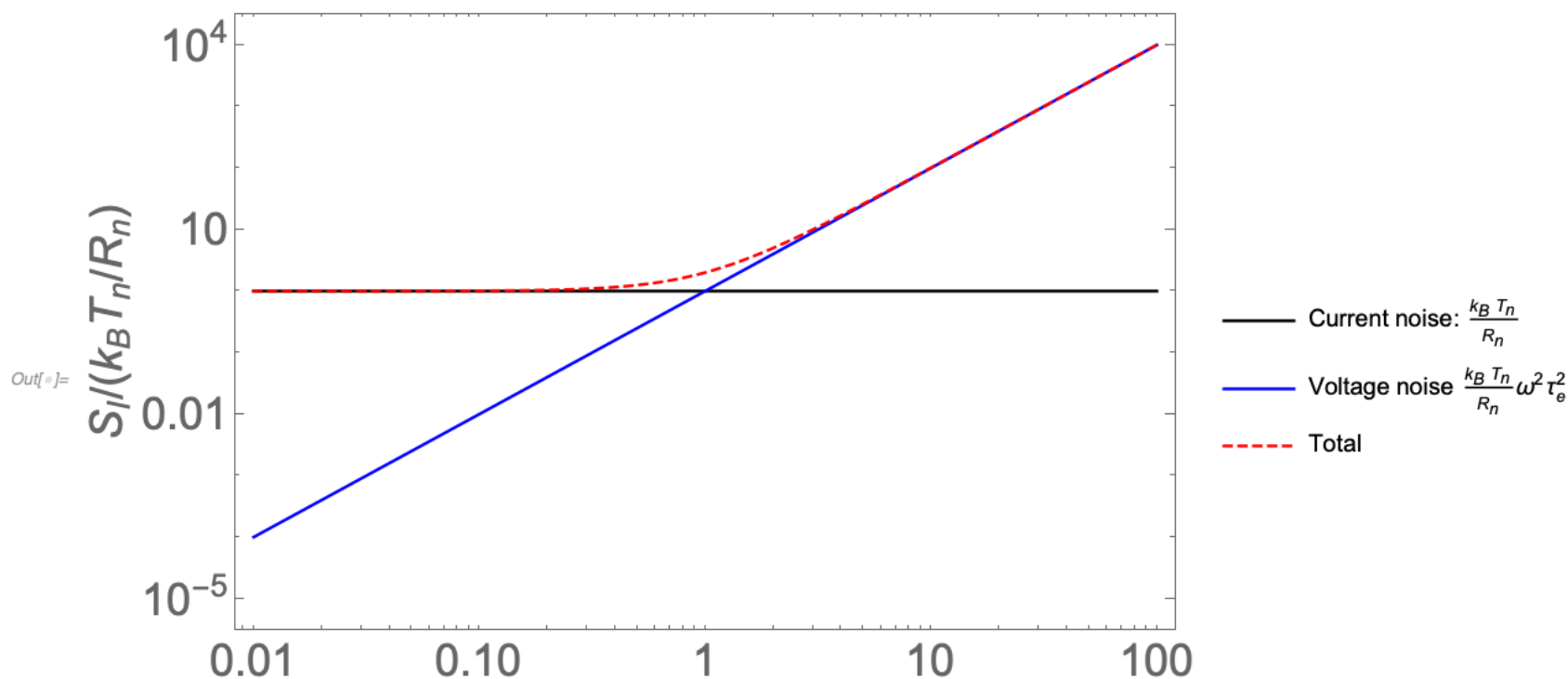- For  $R \rightarrow \infty$   $S_{Io} \rightarrow \frac{k_B T_n}{R_n}$   $\tau_e \rightarrow C R_n$



# The optimum template

- A few additional notes on the exercise

## 2. The filter template.

According to theory, the best estimate is obtained by integrating the data multiplied by a template the Fourier transform of which is

$$h(\omega) = \sigma_e^2 V_i(\omega) / S_{V_n^{in} V_n^{in}}(\omega)$$

From previous calculations

$$h(\omega) = \sigma_e^2 \frac{V_{in}(\omega)}{S_{V_n^{in} V_n^{in}}(\omega)} = \sigma_e^2 \frac{\frac{R}{1+i\omega RC}}{\frac{S_{II} R^2}{1+\omega^2 R^2 C^2} + S_{VV}} = \frac{\sigma_e^2}{R} \frac{1-i\omega RC}{S_{II} + \frac{S_{VV}}{R^2} (1+\omega^2 R^2 C^2)}$$

That can be rewritten as

$$h(\omega) = \frac{\sigma_e^2}{R} \frac{1 - i\omega RC}{S_{Io} (1 + \omega^2 \tau_e^2)}$$